

FIT1047 - Week 3

Central Processing Units, Part 2



MONASH University

Recap

In the previous lecture we saw



- Basic CPU architecture
- MARIE assembly code
- Combinational circuits (in particular: adders)

Overview

- Arithmetic / Logic Units (ALUs)
- Sequential circuits
 - Flip flops, registers, counters
 - memory
- Control
 - Executing a program



Decoders

  Activate one output based on a binary number



Multiplexers

Select one of several inputs

  

Arithmetic Logic Unit (ALU)

ALU

Implements basic computations:

- Integer addition, subtraction (in more complex CPUs: multiplication)
- Comparisons
- Bitwise Boolean operations (AND, OR, NOT)
- Shifting

Inputs:

- Two n -bit **operands**
- Op-code (determines the operation to perform)

Output:

- n -bit result and status flags (overflow? error?)



ALU

How does the circuit decide which operation to perform?

- Simply do all in parallel
- Then choose the result prescribed by the op-code

Sounds like a job for a MUX!

ALU

 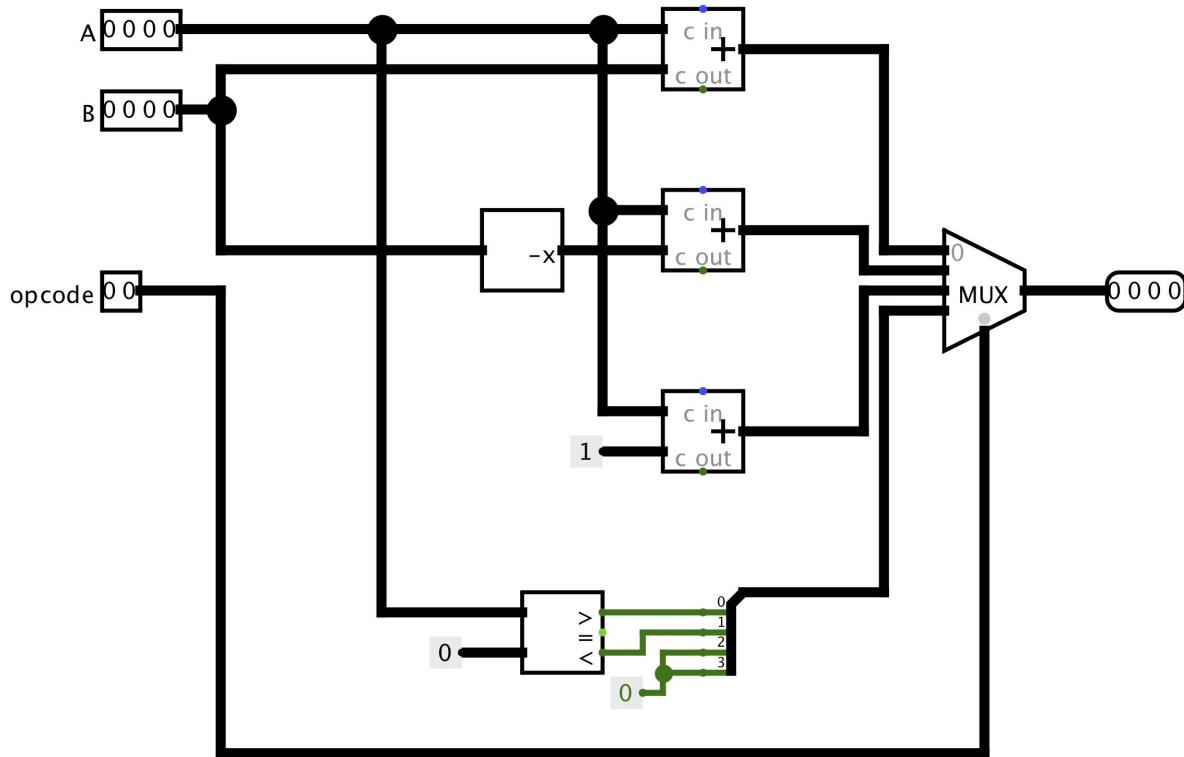


Sequential Circuits

(output depends on *sequence* of inputs)

Sequences


How can a circuit “remember” the past?

Feed the output back into the input!

 


Sequences

Toggle using another input

 


Set/reset latch

 

But digital circuits use a single bit for data!

D flip-flop

 - Two inputs:
 - The bit to be stored
 - A signal: read or write mode
- One output:
 - The bit currently stored




Registers

- Very fast memory inside the CPU
- Some special purpose registers
 - PC, IR, MBR, MAR (for MARIE)
- Some general purpose registers
 - AC (MARIE), AH/AL, BH/BL, CH/CL, DH/DL (x86)
- Fixed bit width
 - E.g. 16 bit in MARIE
 - 16/32 or 64 bits in modern processors


Register file

- Collection of registers
- Each implemented using n flip-flops (for n bits)
- n inputs and outputs
- Additional input: which register to write to
- Additional input: which register to read from

Register file

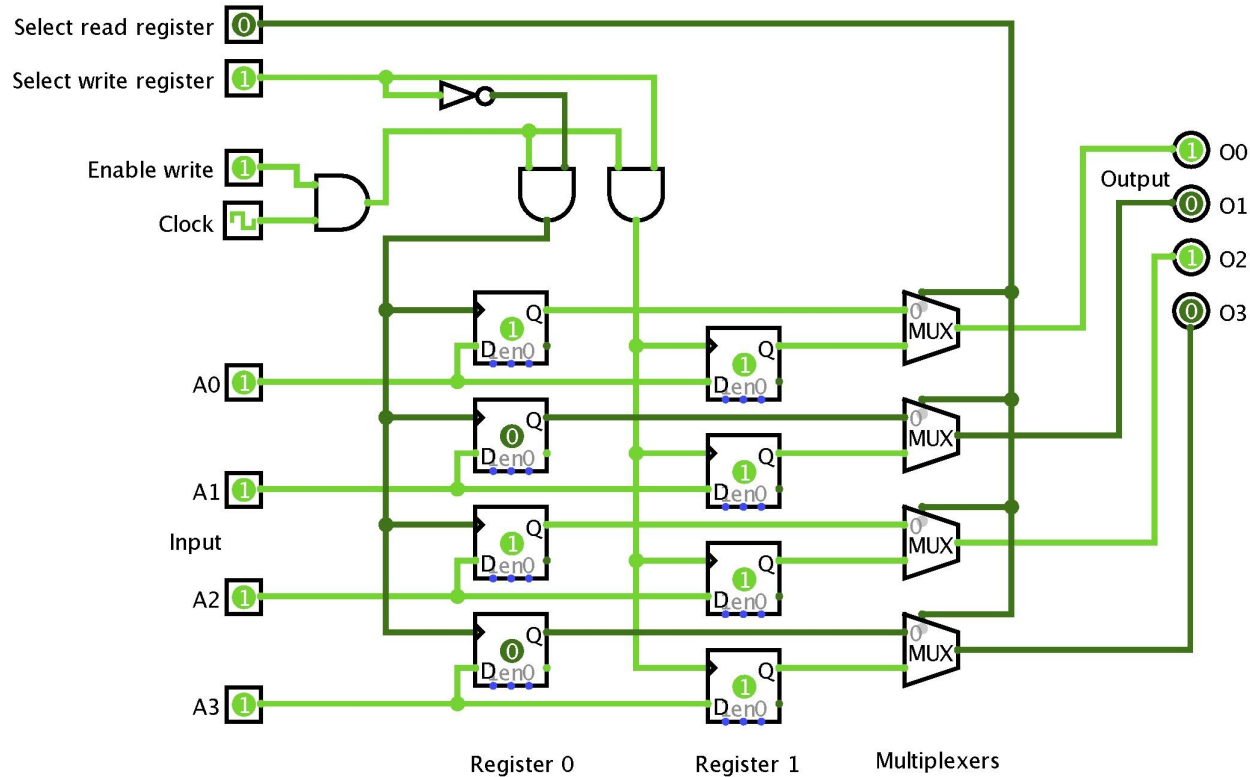

MARIE architecture

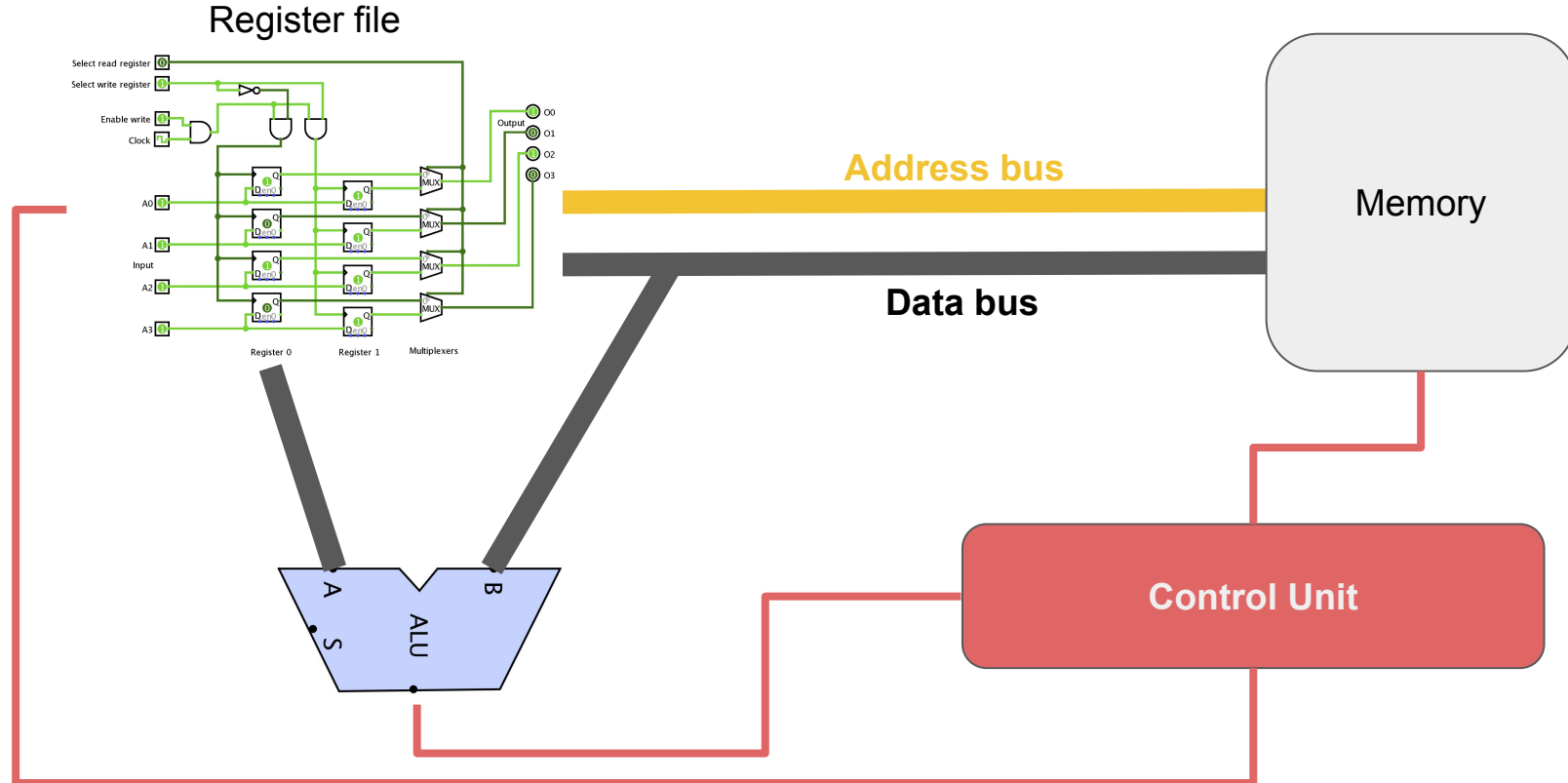

Control Unit

- Controls fetch-decode-execute cycle
- Switches *control signals* on and off:
 - Each signal is a “wire” inside the CPU
 - Which register to read/write
 - Which memory address to read/write
 - Which operation to perform in the ALU
- Needs to “know” which signals to switch on/off for each instruction

Let's specify, for each instruction, what to do!

Register Transfer Language (RTL)

- Break down instructions into small steps
- CPU performs one step per *clock cycle*
- Each step transfers data between registers and/or memory

RTL: fetch

1. **MAR** \leftarrow **PC**
2. **MBR** \leftarrow **M**[**MAR**]
3. **IR** \leftarrow **MBR**
4. **PC** \leftarrow **PC**+1

load PC into memory address register

load value from memory (M) into memory buffer

load value from MBR into instruction register

increment PC to point at next instruction

RTL: decode

- 5. **MAR** \leftarrow **X** *load address X from IR into MAR*
- 6. **MBR** \leftarrow **M[MAR]** *load value from memory into MBR*

Some instruction need both of these steps, some just step 5, some instructions need neither 5 nor 6.

RTL: execute

Depends on the concrete instruction (of course).

Example: Add X

7. **AC** \leftarrow **AC** + **MBR**

(place result of addition in AC)

Example: Jump X

(does not need decode step 6)

6. **PC** \leftarrow **MAR**

(load X, stored in MAR, into PC)

RTL: Full Add X instruction

1. $MAR \leftarrow PC$
2. $MBR \leftarrow M[MAR]$
3. $IR \leftarrow MBR$
4. $PC \leftarrow PC + 1$
5. $MAR \leftarrow X$
6. $MBR \leftarrow M[MAR]$
7. $AC \leftarrow AC + MBR$

Control Signals

Each RTL step tells us which control signals to switch on and off.

Example: $MBR \leftarrow M[MAR]$

(load memory value from address stored in MAR into MBR)

- Switch register file to write into MBR
- Switch memory into read mode

Control Signals

Each RTL step tells us which control signals to switch on and off.

Example: $AC \leftarrow AC + MBR$

(add value in MBR to value stored in AC, store result in AC)

- Switch register file to read from AC
- Switch register file to write into AC
- Switch ALU into “Add” mode (ALU always reads one operand from MBR)

Outlook

Tutorials this week:

- MARIE programming
- Circuits for adding and subtracting

Next lecture:

- More MARIE instructions
- Memory
- Input/Output and Interrupts